

https://www.youtube.com/watch?v=5_ineJpR52s&t=2s

<https://www.youtube.com/watch?v=DQHemB16zbl>

patreon.com/MTECHINDUSTRIES

Testing the latest version of my negative resistance super joule ringer 3.0 circuit & really trying to perfect the negative resistance effect. In this video, I demonstrate how the system can recharge its source 5AH battery/supercap via negative resistance, then run a 120vac inverter for a time. once the inverter is manually switched off with a switch to avoid parasitic power draw the system begins to recharge itself via negative resistance & it's heavy earth grounding connection. The negative resistance effect allows ac loads to be run longer & for the system to rapidly recharge itself. I had 70 watts worth of load running for almost 5 minutes in this video & the system recharged rapidly after manually switching off the AC inverter. Full schematic of this circuit & device will be listed for free on my patreon as a gift to the world & I welcome others to replicate it & see this systems phenomenal effects & capabilities for themselves. below is a full description of the systems construction along with my chat gpt 4.0 conversation & analysis of the system. I had chat gpt analyze my circuit.

ME: Hi, I built a super joule ringer 3.0 circuit on a type 77 metglas laced nickel ferrite nano rod & I'm trying to achieve negative resistance effect within it. It's constructed on a 0.4" by 5.5" ferrite rod. The L1 & L2 coils are centered on the ferrite rod & take up 4 inches of space. Here's the following measurements of the coils.

L2 Coil Wound Second

14AWG

0.297 mH

2.5 PF

0.02 Ohm

L1 Coil Wound First

26AWG

3.01 mH

2.6 PF

1.1 Ohm

48.8 khz is the operating frequency of the system open circuit not under any form of load. I also noticed when I put a resistive load on the system my input power drops. I should also note I connected the output of my super joule ringer 3.0 circuit to a 30k 5 watt carbon film resistor to create an RLC circuit. I then wound a 18 AWG resonant bucking coil over my super joule ringer 3.0 circuit in a transformer fashion with a center tap & it has the following measurements.


18AWG

0.03 mH

2.5 PF

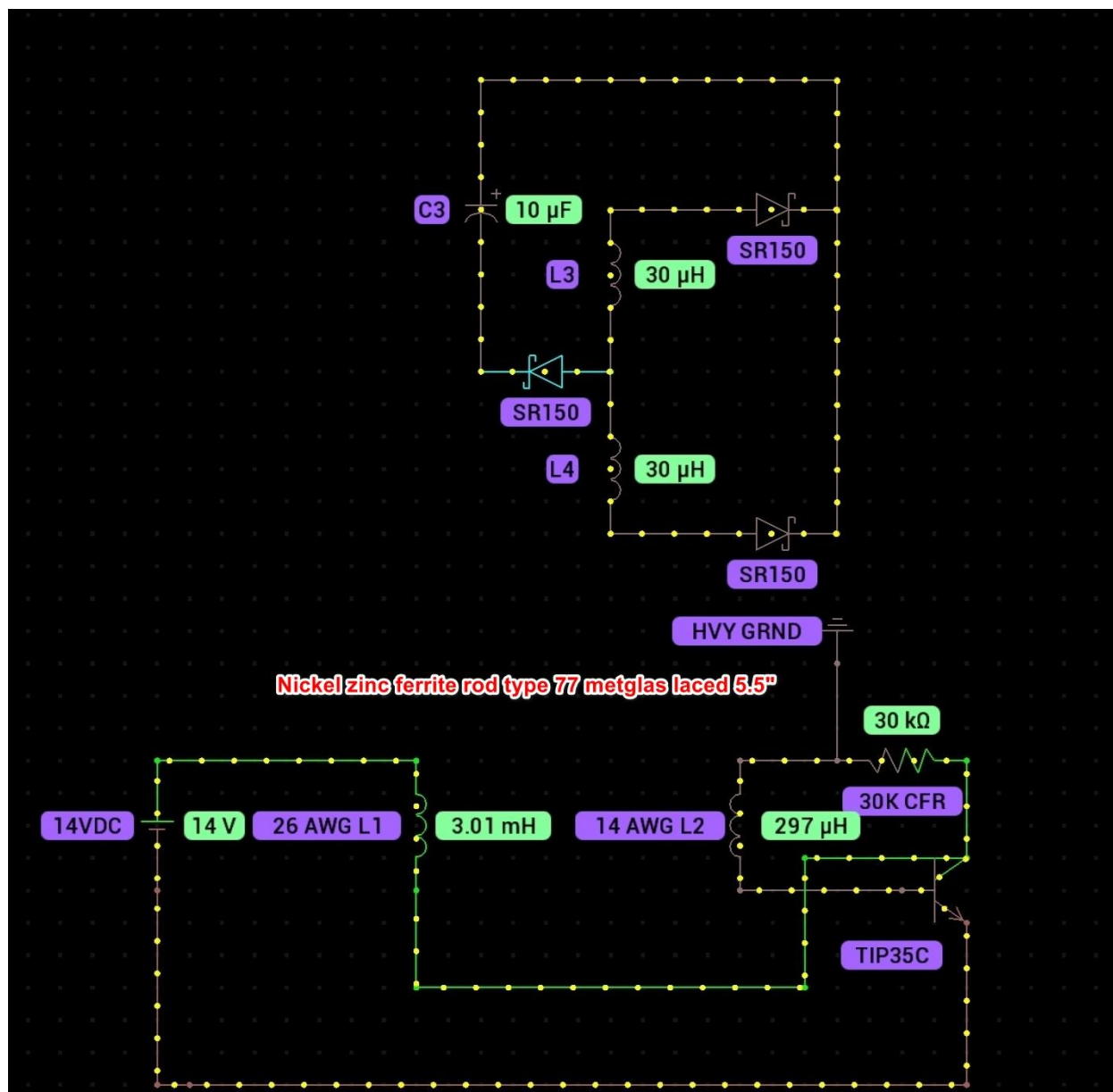0.01 Ohm

I Then Use SR150 Diodes Off Of This Coil To Recharge My Source Battery/Super Capacitor That's Powering My Super Joule Ringer 3.0 Circuit. I Have Three SR150 Diodes Total On This Coil. I Placed One Diode On Each End Of This Bucking Coil Cathode Facing Outward Then I Combined They're Output & The Center Tap Of The Coil Has It's Diode Cathode Facing In.



<https://www.patreon.com/MTECHINDUSTRIES>

Проверяю последнюю версию своей схемы негативного сопротивления супер-джоуль рингера 3.0 и действительно стараюсь довести до совершенства эффект негативного сопротивления. В этом видео я демонстрирую, как система может заряжать свой источник - батарею/суперконденсатор на 5Ач через негативное сопротивление, а затем запускать инвертор 120 В переменного тока на некоторое время. Как только инвертор вручную отключается выключателем для предотвращения паразитного потребления энергии, система начинает заряжаться через негативное сопротивление и ее тяжелое заземление к земле. Эффект негативного сопротивления позволяет увеличить время

работы устройства на переменном токе и быстро зарядить его саму. В этом видео я демонстрирую работу нагрузки 70 Вт в течение почти 5 минут, и система быстро заряжается после ручного отключения инвертора переменного тока. Полная схема этой схемы и устройства будет доступна бесплатно на моем патреоне как подарок миру, и я приглашаю других повторить ее и увидеть феноменальные эффекты и возможности этой системы своими глазами. Ниже приведено полное описание конструкции системы вместе с моим разговором и анализом системы с помощью чата GPT 4.0. Я попросил чат GPT проанализировать мою схему.

Я: Привет, я построил схему супер-джоуль рингера 3.0 на никелевой ферритовой нано-палке типа 77 с метгласом и пытаюсь достичь эффекта негативного сопротивления в ней. Она построена на ферритовой палке размером 0,4 на 5,5 дюйма. Катушки L1 и L2 расположены на центре ферритовой палки и занимают 4 дюйма пространства. Вот измерения катушек:

L2 Катушка, Вторая катушка

14AWG

0,297 мГн

2,5 пФ

0,02 Ом

L1 Катушка, Первая катушка

26AWG

3,01 мГн

2,6 пФ

1,1 Ом

Рабочая частота системы 48,8 кГц при открытой цепи, не подключенной к какой-либо нагрузке. Я также заметил, что когда я подключаю нагрузку к системе, моя входная мощность падает. Следует отметить, что я подключил вывод своей схемы супер-джоуль рингера 3.0 к 30k 5-ваттному углеродному резистору для создания RLC-цепи. Затем я намотал резонансную отводящую катушку 18AWG над моей схемой супер-джоуль рингера 3.0 в виде трансформатора с центральным выводом, и у нее следующие измерения.

18AWG

0,03 мГн

2,5 пФ

0,01 Ом

Затем я использую диоды SR150 от этой катушки для зарядки моей исходной батареи/суперконденсатора, который питает мою схему супер-джоуль рингера 3.0. У меня всего три диода SR150 на этой катушке. Я поставил один диод на каждом конце этой отводящей катушки, катодом наружу, затем я объединил их выход и катод диода от центрального вывода катушки направлен внутрь.